

LABORATORY REPORT - CHAPTER 3

| | |
|---------------------|-----------------|
| Lastname, Firstname | Defne Yaz Kılıç |
| Student ID | 22102167 |
| Date | 9.11.22 |
| Total Grade | /100 |

Remarks: Record all your measurements and write all your answers in the boxes provided.

Preliminary Work

1. Microphone Amplifier

- Consider the TRC-11 microphone amplifier circuit shown in Fig. 1, making use of one of the two OPAMPs in LM358 integrated circuit. Since the OPAMP operates with a single supply voltage, the input DC voltages of the OPAMP should be shifted to a voltage somewhere between V_{CC} and GND. For this purpose, we use the regulated voltage, +6V.

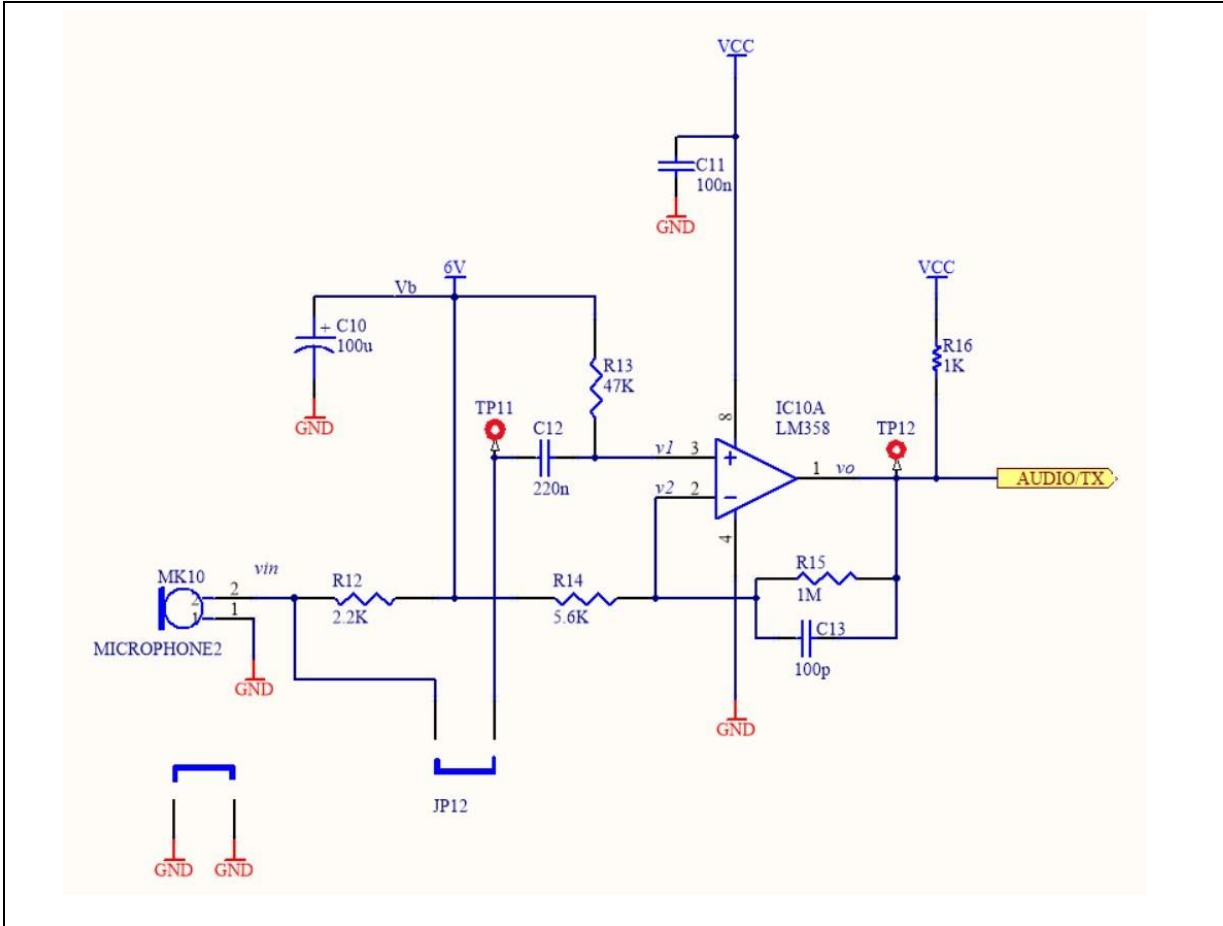


Figure 1: Schematic of microphone amplifier

| Designator | Comment | Description |
|------------|---------|-------------|
|------------|---------|-------------|

| | | |
|------|-------------|---|
| C10 | 100u | Electrolytic Capacitor, 16V |
| C11 | 100n | Capacitor, ceramic disk, 50V |
| C12 | 220n | Capacitor, ceramic disk, 50V |
| C13 | 100p | Capacitor, ceramic disk, 50V |
| IC10 | LM358 | Dual OPAMP |
| MK10 | MICROPHONE2 | Microphone Capsule |
| R12 | 2.2K | Resistor, carbon film, axial leaded, 1/4W |
| R13 | 47K | Resistor, carbon film, axial leaded, 1/4W |
| R14 | 5.6K | Resistor, carbon film, axial leaded, 1/4W |
| R15 | 1M | Resistor, carbon film, axial leaded, 1/4W |
| R16 | 1K | Resistor |

Figure 2: Bill of materials for the microphone amplifier

2. We can find the output voltage, v_o , of this OPAMP circuit using the superposition principle for two sources: A DC source of V_b and an AC source of v_{in} (with a source resistance of R_{12}). First, let us kill the AC source v_{in} and find the output voltage, v_o . Since the capacitor is open-circuit at DC, we write the node equations at v_2 and v_1 as

$$\frac{v_2 - V_b}{R_{14}} + \frac{v_2 - v_o}{R_{15}} = 0 \quad \text{and } v_1 = V_b$$

Assuming that the OPAMP is not saturated, we should have $v_1 = v_2$, and hence we find $v_o = V_b$ (from the datasheet of the OPAMP, we determine that if $0 < v_o < V_{CC} - 2$, the OPAMP is not saturated. Since $V_b < V_{CC} - 2$ our assumption is correct).

Now, we kill the DC source V_b (set $V_b=0$) and assume that the input signal $v_{in}(t)$ is sinusoidal: $v_{in} = V_P \cos(\omega t)$. For this case, we can use the phasors: We write $v_{in} = V_P$. Since the relatively large valued capacitor C_{12} can be assumed a short-circuit and the source resistance, R_{12} is much smaller than R_{13}

$$v_1 = V_P \quad \text{and} \quad \frac{v_2}{R_{14}} + \frac{v_2 - v_o}{R_{15}} = 0$$

Again we assume the OPAMP is not saturated, hence $v_1 = v_2 = V_P$. Now, we find

$$v_o = \left(1 + \frac{R_{15}}{R_{14}}\right) V_P$$

We note that the OPAMP acts like a non-inverting amplifier of voltage gain

$$A_v = \left(1 + \frac{R_{15}}{R_{14}}\right)$$

Using superposition, the output voltage is

$$v_o = V_b + A_v V_P$$

The output is equal to an amplified version of the input AC signal shifted by V_b . Calculate the value of voltage gain, A_v , from the resistor values.

Because of C12 and R13, the gain decreases at frequencies lower than the corner frequency of

$$f_1 = \frac{1}{2\pi R_{13}C_{12}}$$

Because of C13 and R15, the gain decreases at frequencies higher than the corner frequency of

$$f_2 = \frac{1}{2\pi R_{15}C_{13}}$$

Calculate these frequencies.

$$A_v = 179.6$$

$$f_1 = 15.42 \text{ Hz}$$

$$f_2 = 1.58 \text{ kHz}$$

1.2. GRADE:

3. The gain function in decibels is plotted in Fig. 3. If $f_1 \ll f \ll f_2$, then $|v_o/v_{in}| = A_v =$

$20\log_{10}A_v = A_{v\text{dB}}$. If $f = f_1$ or $f = f_2$, then $|v_o/v_{in}| = A_v/\sqrt{2} = A_{v\text{dB}} - 3\text{dB}$ (3 dB less than the low frequency value).

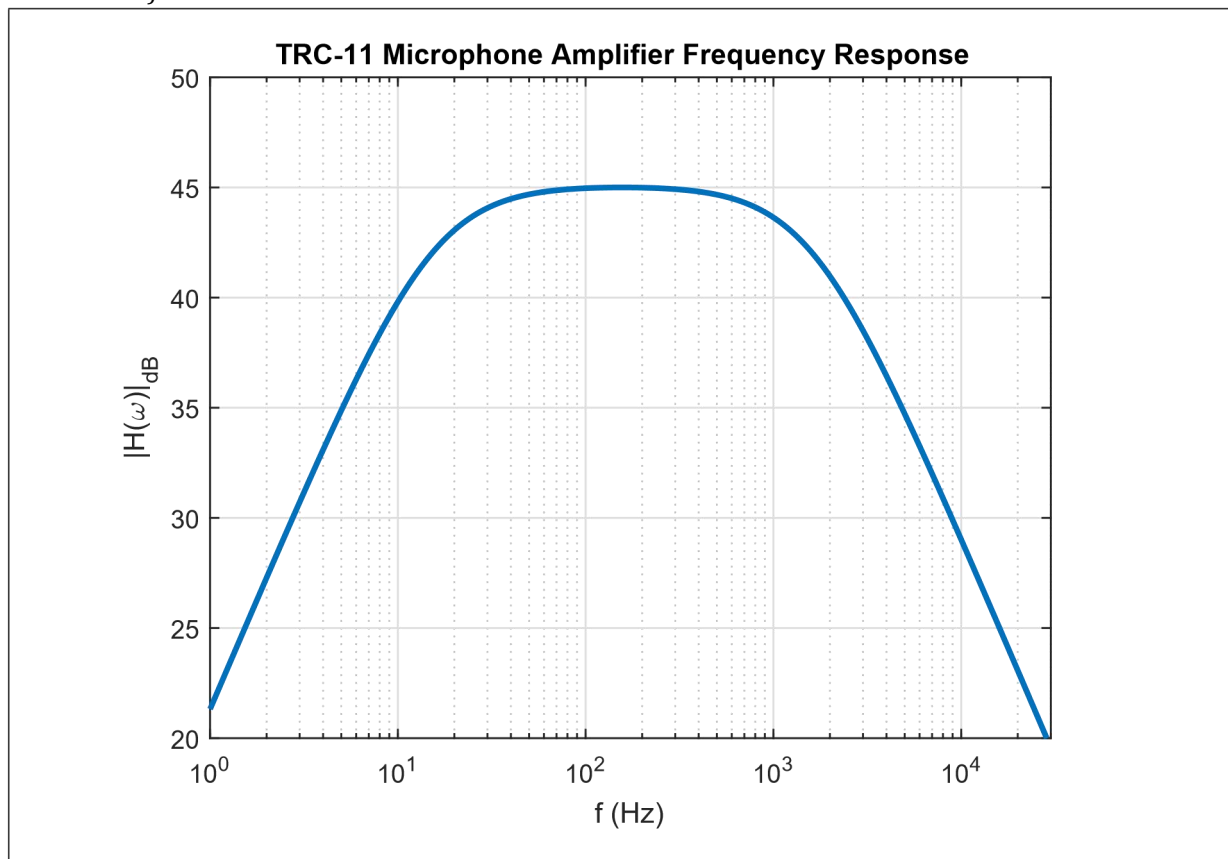


Figure 3: Calculated Frequency Response of the Microphone Amplifier

The MATLAB code to plot this function is

```
% MATLAB code to plot the transfer function %
% of the Microphone amplifier clear all % clear all
variables in MATLAB hold off
```

```

fmin=1; %minimum frequency in Hz
fmax=30e3; %maximum frequency in Hz C12=220e-
9; % C12 capacitor value in F
C13=100e-12; % C13 capacitor value in F
R13=47e3; % R13 resistance in Ohms
R15=1000e3; % R15 resistance in Ohms
R14=5.6e3; % R14 resistance in Ohms Av=1+R15/R14;


f=fmin:fmin/5:fmax; % Frequency vector w=2*pi*f; %
angular frequency vector
H=Av./((1+j*w*R15*C13).*(1+j./(w*C12*R13)));
% MATLAB performs an array operation
% Note that we need a "." in front of operators
% to perform array operations
Hdb=20*log10(abs(H)); % calculate the magnitude of
% the transfer function in dB

semilogx(f,Hdb,'LineWidth',2) % plot on a logarithmic x-axis
% with a linewidth of 2 grid on % to plot the grid lines xlabel('f (Hz)') %
to place the x-label on the plot ylabel('|H(\omega)|_{dB}') % to place
the y-label title('TRC-11 Microphone Amplifier Frequency Response')
% to place a title hold on
axis([fmin fmax 20 50]); % define the axes limits

```

Find the value of the resistor R_{15} to have a mid-band gain of $A_v=40$ dB. Plot the corresponding frequency response using the modified MATLAB code.

| |
|---------------------------------|
| $R_{15}= 554.4 \text{ K}\Omega$ |
|---------------------------------|

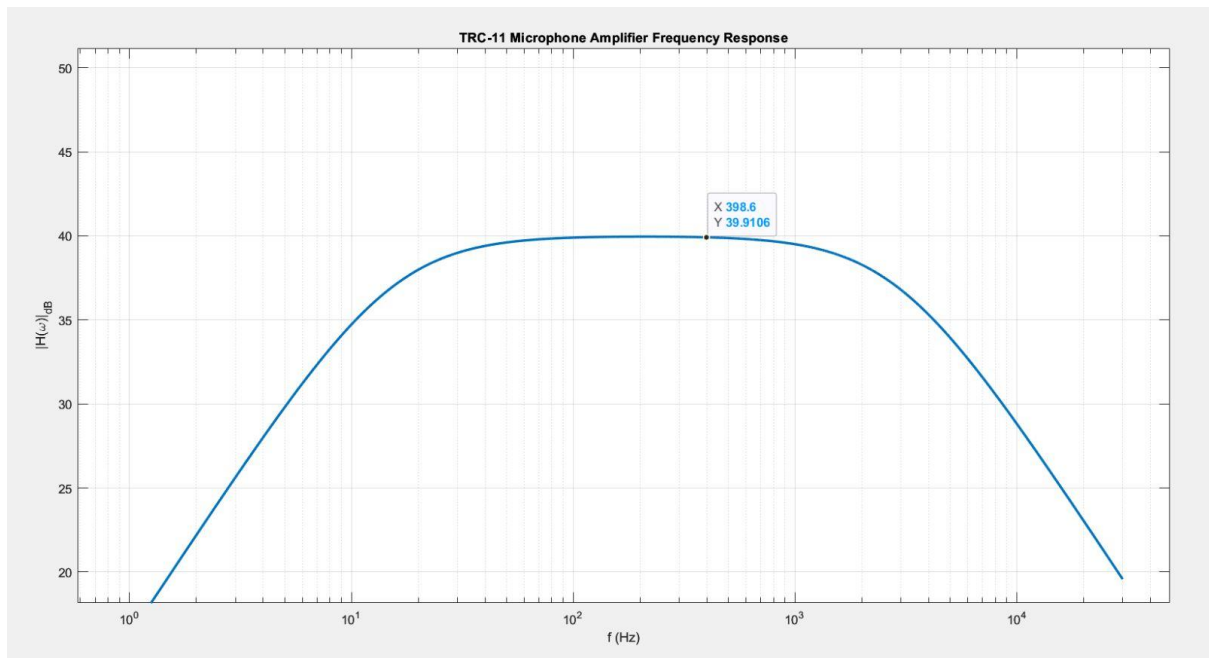

1.3. GRADE:

4. From the datasheet of the OPAMP LM358 on page 355, the typical gain factor A of the OPAMP is found as 110 dB. What is this amplifier's approximate supply current, I_S , from +12 V supply? What is the open-loop voltage gain, A_0 , at 10 kHz in dB (page 355)?

$I_S = 0.75 \text{ mA}$

$A_0 = 40 \text{ dB}$

1.4. GRADE:

2. Loudspeaker/Earphone Amplifier

1. A schematic diagram of the loudspeaker amplifier is given in Fig. ??.

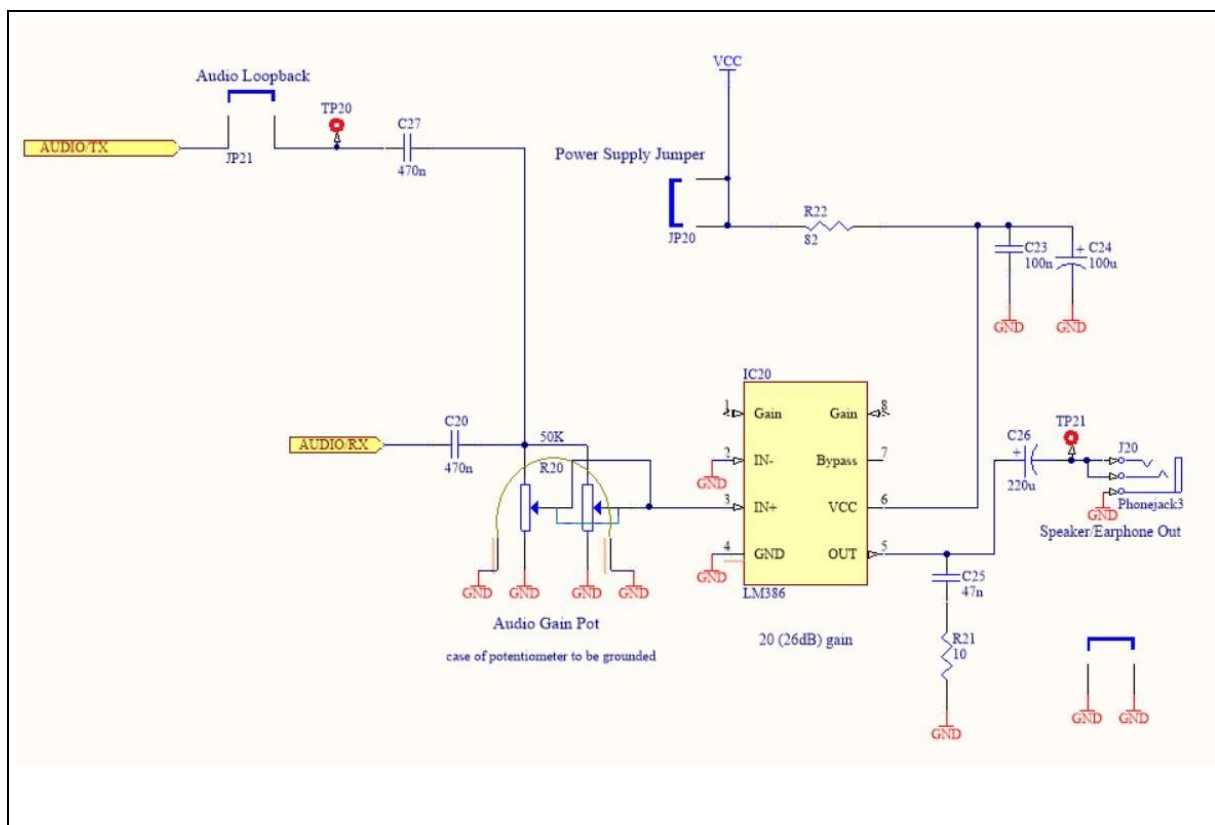


Figure 4: Schematic of the loudspeaker/earphone amplifier

- IC20 is (LM386) a low-voltage audio amplifier integrated circuit. Examine the datasheet given on page 357. Which type of package is your integrated circuit? What is the supply voltage range of this IC?

| | |
|---------------------|-------|
| Package type | DIP-8 |
| Min. Supply voltage | 4V |
| Max. Supply voltage | 12V |

2.2. GRADE:

| Designator | Comment | Description |
|------------|------------|----------------------------------|
| C20, C27 | 470n | Capacitor, ceramic disk, 50V |
| C23 | 100n | Capacitor, ceramic disk, 50V |
| C24 | 100u | Electrolytic Capacitor, 16V |
| C25 | 47n | Capacitor, ceramic disk, 50V |
| C26 | 220u | Electrolytic Capacitor, 16V |
| IC20 | LM386 | Low Voltage Audio amplifier |
| J20 | Phonejack3 | Speaker/Earphone jack, PCB mount |
| R20 | 50K | Potentiometer, Stereo |

| | | |
|-----|----|---|
| R21 | 10 | Resistor, carbon film, axial leaded, 1/4W |
| R22 | 82 | Resistor, carbon film, axial leaded, 1/4W |